

CURRENT
ELECTRICITY

SUB TOPICS

* * *



Represents conducting wire where Potential difference Same

Same Potential.

Put a Random Variable (A) For Simplification...

- ⇒ Ohm's Law
- ⇒ Conductor
- ⇒ Electric current
 - (i) Instantaneous
 - (ii) Average current
- ⇒ Current density (J)
- ⇒ Parallel and Series connections.
- ⇒ Kirchhoff's Law
- ⇒ EMF...
- ⇒ Average relaxation time ($\bar{\tau}$)
- ⇒ Mobility (μ)
- ⇒ Efficiency of Cell (η)
- ⇒ Power Rating of Bulbs
- ⇒ Equivalent Resistance by Method of Symmetry
- ⇒ Meter Bridge Experiment.
- ⇒ Wheatstone Bridge
- ⇒ Electrical Power consumption
- ⇒ Max Power Transfer theorem
- ⇒ N identical cells
 - (i) Series
 - (ii) Parallel.
- ⇒ Potentiometer, Galvanometer
- ⇒ Conversion of Galvanometer into a Voltmeter in Range (0-V) volts
- ⇒ Amount of Resistance given to Shunt...

CONCEPTS

And

KEY POINTS :

$$* i = \frac{dq}{dt}$$

$$* q = \int i dt$$

$$* i_{avg} = \frac{\int_{t_1}^{t_2} i dt}{t_2 - t_1}$$

$$* \text{Ohm's Law: } \boxed{V = iR}$$

Current density (J):

$$J = \frac{i}{A} \text{ Amp/m}^2 = \alpha E$$

$$J = \frac{n e A V_d}{A} = n e V_d$$

$$\boxed{i = n e A V_d} \sim \text{General Current formula}$$

$$\alpha : \text{conductivity} = \frac{J}{E}$$

ρ : Resistivity

$$\rho = \frac{1}{\alpha}$$

$$\text{Mobility} (\mu) = \frac{V_d}{E}$$

$$\Rightarrow \boxed{\alpha = n e \mu}$$

$$\Rightarrow V_d = \left(\frac{e E}{m} \right) \tau \quad (\because \tau \text{ is average relaxation time})$$

$$\Rightarrow \alpha = \frac{n e^2 \tau}{m}$$

Resistance:

$$R = \frac{\rho l}{A}$$

Specific resistance is Same for two diff
Bodies of Same Material ...

ρ is independent on diameter ... //

* Parallel :

- (i) $\rightarrow$ Diff
- (v) $\rightarrow$ Same

* Series ,


- (i) $\rightarrow$ Same
- (v) $\rightarrow$ Different ... "

□ Electrical Power consumption:


$P_{xt} = \text{Heat transfer}$

$$P_{xt} = ms\Delta T$$


□ Terminal P.D.

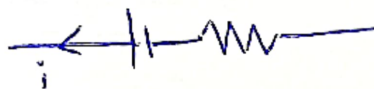


i. $V_A - V_B = E - ir$

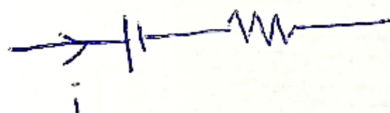

ii. $V_A - V_B = E + ir$

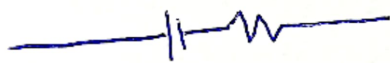

iii. $V_A - V_B = E$ ($\because i=0$)

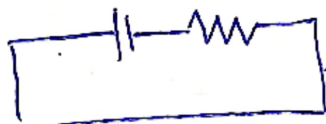

Pure conducting wire.

iv. $V_A - V_B = 0$

$$1. \quad S = \frac{i_g G}{I - i_g}$$

$$2. \quad i_g (G + S) = V$$

Converting Moving Coil Galvanometer into an


Ammeter of Range (0-I) Amp.

Volt Meter of Range (0-V) Volt

Low Imp in Parallel
High Imp in Series

CURRENT ELECTRICITY ...

Conductor

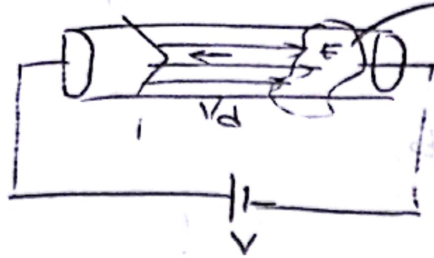


electron cloud

$$i = neAv_d$$

$$J = \frac{i}{A} = nev_d$$

$$J = \sigma E \quad (\because \sigma = \text{conductivity})$$
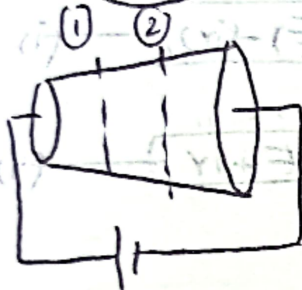
$$\sigma = \frac{1}{\rho} \quad \text{Resistivity ...}$$



$$i_1 = i_2$$

$$J_1 > J_2$$

$$V_{d1} > V_{d2}$$

$$E_1 > E_2$$

Mobility (μ)

$$\mu = \frac{v_d}{E}$$

$$\sigma = ne\mu$$

Mobility

Charge of each electron ...

No. of e^-

$$\sigma = \frac{ne^2\tau}{m}$$

Relaxation time

Time interval

Blue

Collisions to Collision

Uniform Conductor:



$$J = \sigma E$$


$$\frac{i}{A} = \frac{1}{\rho} \frac{V}{l}$$

$$\left(\frac{\rho}{A}\right)l = R$$

$$V = iR$$

$$R = \frac{\rho l}{A}$$

1.

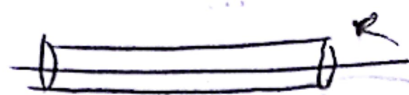

$$R = \frac{\rho l}{A} = \frac{\rho l}{\pi R^2}$$


2.




$$R = \frac{\rho l}{\pi ab}$$

$V_{AB} = 1$
 $\frac{1}{A} = \frac{1}{\pi R^2}$


SL

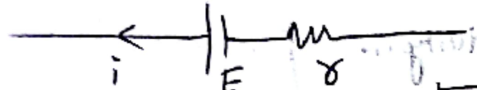


$$V = (E) - (ir)$$

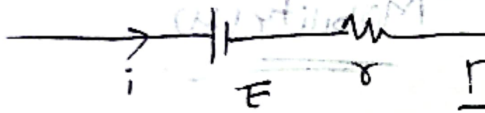

$$V = E + ir$$

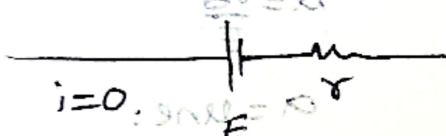

$$V = E$$

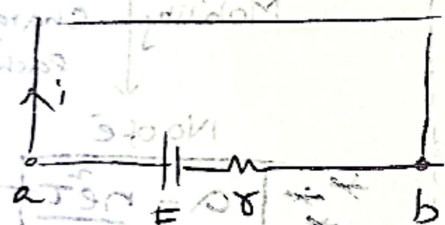


$$V = 0$$

let $V = V_a - V_b = \text{Terminal Potential Drop} \dots$

Grouping of cells:

- i. Parallel
- ii. Series

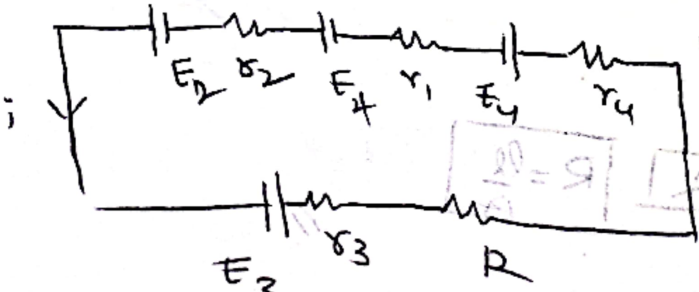

$$i = \frac{E_1 + E_2 + E_3 + E_4}{R + r_1 + r_2 + r_3 + r_4}$$

$$10 = 17$$

8. n identical cells:


$$E = 10V, r = 2\Omega$$

Out of 10 cells 3 cells are

connected by reverse.

Polarity...

$$70 - 30 = \frac{40}{20} = 2$$

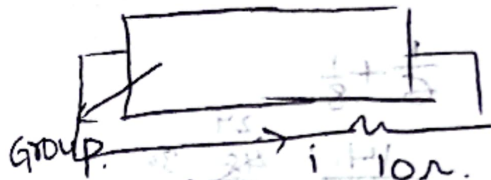


$$V = iR$$

$$i = \frac{V}{R} = \frac{2}{10} = \frac{1}{5}$$

$$i = \frac{4}{3}A$$

Parallel Grouping of cells:

1.

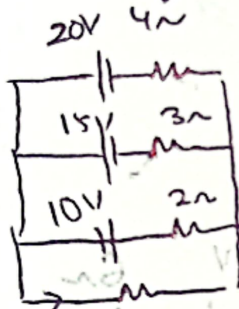

$$R = 6\Omega$$

find $i = ?$

$$\frac{1}{4} + \frac{1}{3} + \frac{1}{2} = \frac{1}{2}$$

$$\frac{3}{4} + \frac{1}{3}$$

$$\frac{13}{12} = \frac{12}{13}$$

$$i = \frac{\sum E}{r}$$

$$1 + R \sum \frac{1}{r}$$

$$1 + 6\left(\frac{1}{4} + \frac{1}{3} + \frac{1}{2}\right)$$

$$20 - 4i = \frac{2}{3} \times 6$$

$$= 4$$

$$\frac{5}{15} = \frac{2}{3}$$

$$\frac{15}{12} = \frac{13}{7}$$

$$0 = 10 + 15 - 3i = 4$$

$$3i = 11$$

$$-10 + 2i = -4$$

$$2i = 6$$

$$i = 3$$

Points related Questions

$$dw = Fdx \quad \text{--- (1)}$$

$$dw = P \cdot A dx$$

$$dw = P \cdot dV$$


$$\frac{dw}{dV} = P$$

$$W = \int_{x_1}^{x_2} F dx$$

$$dx = V dt$$

$$a = V \frac{dx}{dt}$$

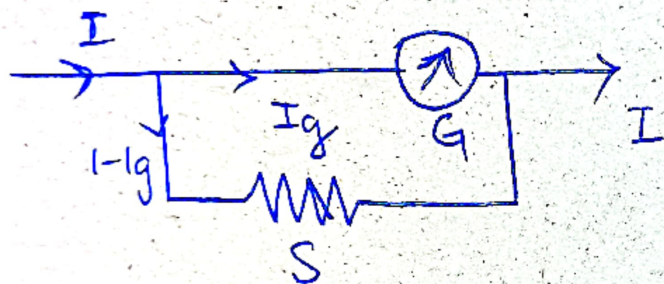Derive by Equations and
Get the Relation...



$$I_g G = (I - I_g) S$$

$$S = \frac{I_g G}{(I - I_g)} \quad \text{--- (1)}$$

Where

- i. $S \rightarrow$ Shunt resistance.
- ii. $G \rightarrow$ Galvanometer coil in Ohm $\sim$
- iii. $I \rightarrow$ Measure Current in Amp (A)
- iv. $I_g \rightarrow$ Mostly in mA